

Current Electricity

Solⁿ 1.

$$\mathcal{E} = 12 \text{ V}$$

$$r = 0.4 \Omega$$


$$I_{\text{max}} = ?$$

$$I = \frac{\mathcal{E}}{R+r}$$

$$I_{\text{max}} = \frac{\mathcal{E}}{r} \quad [R=0]$$

$$= \frac{120}{0.4} = 30$$

$$I_{\text{max}} = 30 \text{ A}$$

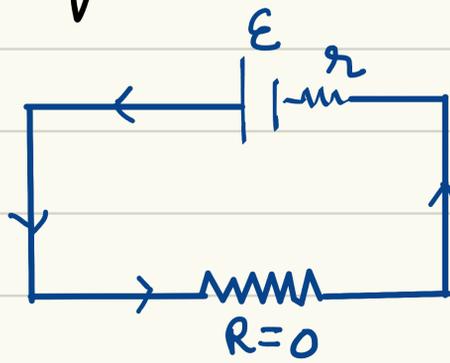

Solⁿ

$$\mathcal{E} = 10 \text{ V}$$

$$r = 3 \Omega$$

$$R = ?$$

$$I = 0.5 \text{ A}$$

$$V = ?$$

$$I = \frac{\mathcal{E}}{R+r}$$

$$R+r = \frac{\mathcal{E}}{I} = \frac{100}{0.5} = 20$$

$$R+r = 20$$

$$R = 20 - r$$

$$= 20 - 3$$

$$R = 17 \Omega \text{ Ans}$$

Now, terminal voltage

$$V = \mathcal{E} - Ir$$

$$= 10 - (0.5 \times 3)$$

$$= 10 - 1.5$$

$$V = 8.5 \text{ volt} \quad \text{Ans}$$

Solⁿ

$$R_T = R_0 (1 + \alpha \Delta T) \quad [\Delta T = T_2 - T_1]$$

$$R_2 = R_1 (1 + \alpha \Delta T)$$

Given

$$T_1 = 27^\circ\text{C}$$

$$T_2 = ?$$

$$R_1 = 100 \Omega$$

$$R_2 = 117 \Omega$$

$$\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

We know

$$\alpha = \frac{R_2 - R_1}{R_1 \Delta T}$$

$$\text{or } \Delta T = \frac{R_2 - R_1}{R_1 \alpha}$$

$$= \frac{117 - 100}{100 \times 1.7 \times 10^{-4}}$$

$$= \frac{170 \times 10^2}{1.7}$$

$$= 10^3 = 1000^\circ\text{C}$$

$$\Delta T = 1000$$

$$T_2 - T_1 = 1000$$

$$T_2 = 1000 + T_1$$

$$= 1000 + 27$$

$$\text{or } T_2 = 1027^\circ\text{C}$$



Solⁿ

Given

$$l = 15 \text{ m}$$

$$A = 6 \times 10^{-7} \text{ m}^2$$

$$R = 5.0 \Omega$$

$$\rho = ?$$

$$\rho = \frac{RA}{l}$$

$$= \frac{5 \times 6 \times 10^{-7}}{15}$$

$$\rho = 2 \times 10^{-7} \Omega \text{ m}$$

Ans

Solⁿ

$$R_1 = 2.1 \Omega$$

$$T_1 = 27.5^\circ \text{C}$$

$$R_2 = 2.7 \Omega$$

$$T_2 = 100^\circ \text{C}$$

$$\alpha = ?$$

We have

$$\alpha = \frac{R_2 - R_1}{R_1 \Delta T}$$

$$= \frac{2.7 - 2.1}{2.1 \times (100 - 27.5)}$$

$$= \frac{0.6}{24 \times 72.5}$$

$$= \frac{2}{7 \times 72.5}$$

$$= \frac{2}{507.5}$$

$$\alpha = \frac{800}{\frac{20000 \times 10^{-3}}{5075}}$$
$$= \frac{800 \times 10^{-3}}{203}$$

[Multiply by $10^3 \times 10^{-3}$ to make calculation easy]

$$\alpha = 3.94 \times 10^{-3}$$
$$= 0.00394$$
$$\alpha = 0.0039 \text{ } ^\circ\text{C}^{-1}$$

Ans →

Jyoti Sharma Physics

Solⁿ 6

Given

$$V = 230 \text{ volt}$$

$$I_1 = 3.2 \text{ A}$$

$$I_2 = 2.8 \text{ A}$$

$$T_1 = 27^\circ\text{C}$$

$$\alpha = 1.70 \times 10^{-4} \text{ }^\circ\text{C}^{-1}$$

$$T_2 = ?$$

We have

$$R_2 = R_1 (1 + \alpha \Delta T)$$

$$\text{here } R_1 = \frac{V}{I_1} = \frac{230}{3.2} \Omega$$

$$\text{and } R_2 = \frac{V}{I_2} = \frac{230}{2.8} \Omega$$

$$\text{so } \frac{230}{2.8} = \frac{230}{3.2} (1 + \alpha \Delta T)$$

$$\frac{8}{7} = 1 + \alpha \Delta T$$

$$\frac{8}{7} - 1 = \alpha \Delta T$$

$$\frac{1}{7} = \alpha \Delta T$$

$$\Delta T = \frac{1}{7\alpha} = \frac{1}{7 \times 1.7 \times 10^{-4}}$$

$$\Delta T = \frac{1}{11.9 \times 10^{-4}} = \frac{10^4}{11.9}$$

$$= \frac{1000 \times 10^2}{11.9}$$

$$\Delta T = 8.40 \times 10^2$$

$$T_2 - T_1 = 840$$

$$T_2 = 840 + T$$


$$= 840 + 27$$

$$T = 867^\circ\text{C}$$

Ans

i.e at 867°C the current becomes 2.8 A

Solⁿ 7

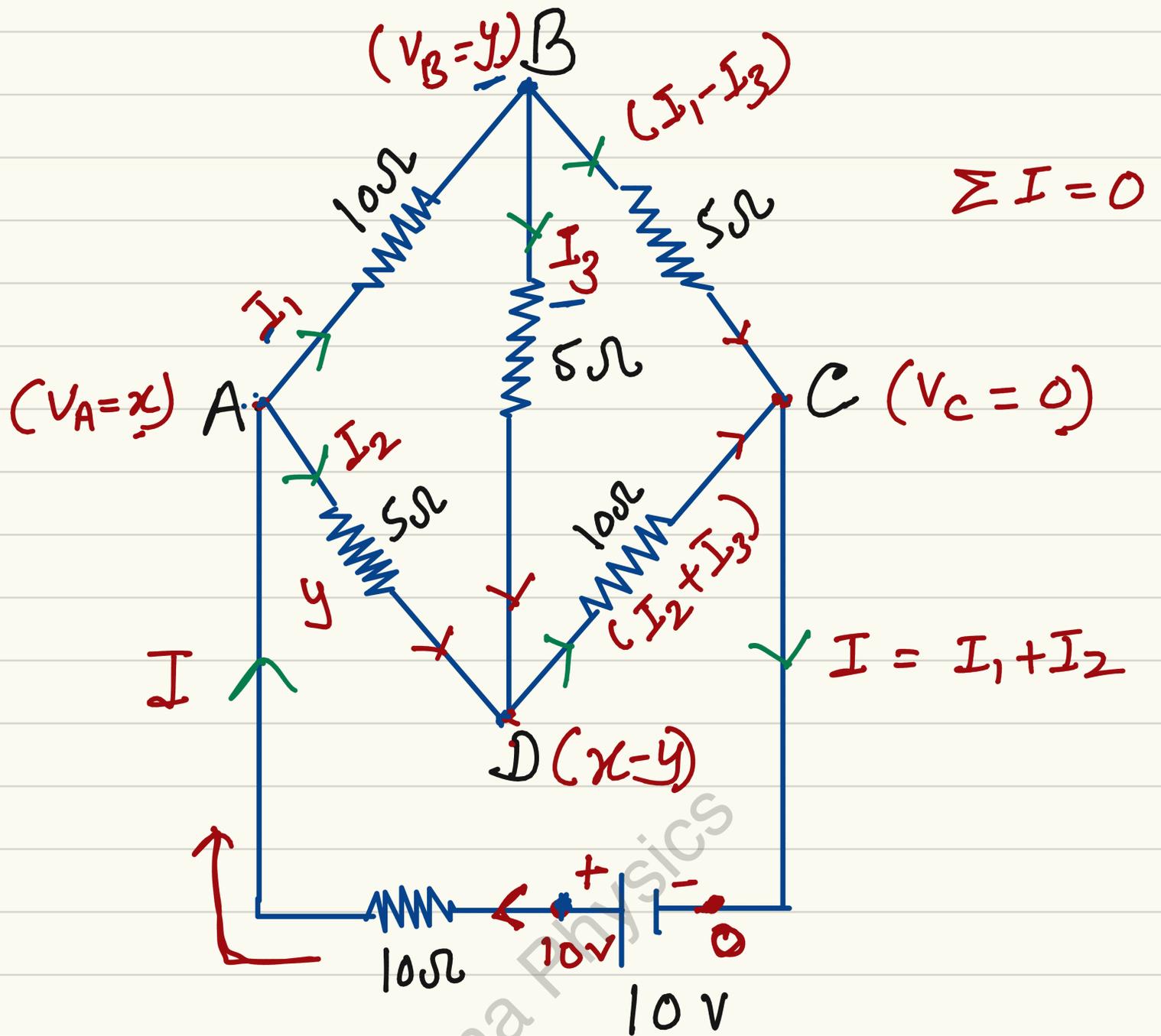

By KCL, at point 'A'

$$I = I_1 + I_2$$

By Ohm's law

$$I = \frac{V}{R}$$

put the values

$$\frac{10-x}{10} = \frac{x-y}{10} + \frac{y}{5}$$

$$\text{or } 10-x = x-y + 2y$$

$$\text{or } 10-x = x+y$$

$$\text{or } 2x + y = 10 \quad \text{--- (1)}$$

At point 'B'

$$I_1 = I_3 + (I_1 - I_3)$$

$$\frac{x-y}{10} = \frac{y-(x-y)}{5} + \frac{y}{5}$$

$$\text{or } \frac{x-y}{10} = \frac{2y-x}{5} + \frac{y}{5}$$

$$\text{or } x-y = 2(2y-x) + 2y$$

$$\text{or } x-y = \underline{4y} - 2x + \underline{2y}$$

$$3x = 7y$$

$$\text{or } y = \frac{3x}{7}$$

put $y = \frac{3x}{7}$ in eqⁿ (1),

$$2x + y = 10$$

$$2x + \frac{3x}{7} = 10$$

$$14x + 3x = 70$$

$$17x = 70$$

$$x = \frac{70}{17} \text{ volt}$$

$$\text{so } y = \frac{3x}{7} = \frac{3}{7} \times \frac{70}{17}$$

$$= \frac{3}{7} \times \frac{70}{17}$$

$$y = \frac{30}{17}$$

We have,

$$x = \frac{70}{17} \text{ volt}, \quad y = \frac{30}{17} \text{ volt}$$

Therefore by,

$$I_1 = \frac{x-y}{10} = \frac{\frac{70}{17} - \frac{30}{17}}{10}$$

$$\text{or } I_1 = \frac{40}{17 \times 10}$$

$$\text{or } I_1 = \frac{4}{17} \text{ Amp}$$

Now

$$I = \frac{10-x}{10}$$

$$= \frac{10 - \frac{70}{17}}{10}$$

$$= \frac{100}{17 \times 10} = \frac{10}{17}$$

i.e

$$I = \frac{10}{17} \text{ Amp}$$

Now

$$I_2 = I - I_1$$

$$= \frac{10}{17} - \frac{4}{17} = \frac{6}{17}$$

$$\text{i.e } I_2 = \frac{6}{17} \text{ Amp}$$

Now,

$$I_3 = \frac{y - (x-y)}{5} = \frac{2y-x}{5}$$

$$= \frac{2 \times \frac{30}{17} - \frac{70}{17}}{5}$$

$$I_3 = \frac{10}{17 \times 5} = \frac{-2}{17}$$

$$\therefore I_3 = -\frac{2}{17} \text{ Amp}$$

So current in branch

$$AB = I_1 = \frac{4}{17} \text{ A}$$


$$AD = I_2 = \frac{6}{17} \text{ A}$$

$$BD = I_3 = -\frac{2}{17} \text{ A}$$

$$BC = I_1 - I_3 = \frac{6}{17} \text{ A}$$

$$DC = I_2 + I_3 = \frac{4}{17} \text{ A}$$
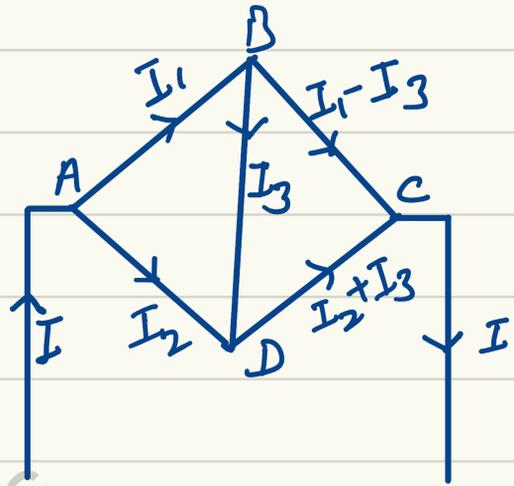
$$\text{Total current } I = \frac{10}{17} \text{ A} \quad \underline{\text{Ans}}$$



Jyoti Sharma Physics

II Method

By KCL

$$I = I_1 + I_2$$

By KVL ($\sum V = \sum IR = 0$)

In loop ①

$$-10I_1 - 5I_3 + 5I_2 = 0$$

$$\text{or } -2I_1 - I_3 + I_2 = 0$$

$$\text{or } 2I_1 - I_2 + I_3 = 0 \quad \text{--- (1)}$$

In loop ②

$$-5I_3 - 10(I_2 + I_3) + 5(I_1 - I_3) = 0$$

$$\text{or } -5I_3 - 10I_2 - 10I_3 + 5I_1 - 5I_3 = 0$$

$$\text{or } 5I_1 - 10I_2 - 20I_3 = 0$$

$$\text{or } -I_1 + 2I_2 + 4I_3 = 0 \quad \text{--- (2)}$$

In loop ③ (ADCA)

$$-5I_2 - 10(I_2 + I_3) + 10 - 10I_1 = 0$$

$$\text{or } -5I_2 - 10I_2 - 10I_3 + 10 - 10(I_1 + I_2) = 0$$

$$\text{or } -25I_2 - 10I_3 - 10I_1 + 10 = 0$$

$$2I_1 + 5I_2 + 2I_3 = 2 \quad \text{--- (3)}$$

We have

$$\begin{array}{l} I_1 \left[\begin{array}{l} 2I_1 - I_2 + I_3 = 0 \quad \text{--- (1)} \\ -I_1 + 2I_2 + 4I_3 = 0 \quad \text{--- (2)} \\ 2I_1 + 5I_2 + 2I_3 = 2 \quad \text{--- (3)} \end{array} \right. \end{array}$$

eqⁿ (1) + 2x eqⁿ (2)

$$\begin{array}{r} 2I_1 - I_2 + I_3 = 0 \\ -2I_1 + 4I_2 + 8I_3 = 0 \\ \hline \end{array}$$

$$3I_2 + 9I_3 = 0$$

$$\text{or } I_2 + 3I_3 = 0$$

$$\text{or } \boxed{I_2 = -3I_3}$$

Again

2x eqⁿ (2) + eqⁿ (3)

$$-2I_1 + 4I_2 + 8I_3 = 0$$

$$2I_1 + 5I_2 + 2I_3 = 2$$

$$\hline 9I_2 + 10I_3 = 2$$

here we put $I_2 = -3I_3$, we get

$$9(-3I_3) + 10I_3 = 2$$

$$\text{or } -27I_3 + 10I_3 = 2$$

$$-17I_3 = 2$$

So

$$I_3 = -\frac{2}{17} \text{ A}$$

$$I_2 = -3 I_3$$

$$= -3 \times \left(-\frac{2}{17}\right)$$

$$I_2 = \frac{6}{17} \text{ A}$$

From eqⁿ ①

$$2I_1 - I_2 + I_3 = 0$$

$$2I_1 - \frac{6}{17} - \frac{2}{17} = 0$$

$$2I_1 = \frac{8}{17}$$

$$I_1 = \frac{4}{17} \text{ A}$$

$$I_2 = \frac{6}{17} \text{ A}$$

$$I_3 = -\frac{2}{17} \text{ A}$$

Ans

Solⁿ 8.

Given


$$E = 8V$$

$$r = 0.5\Omega$$

$$R = 15.5\Omega$$

$$V_{\text{ext}} = 120V$$

$$V = ?$$

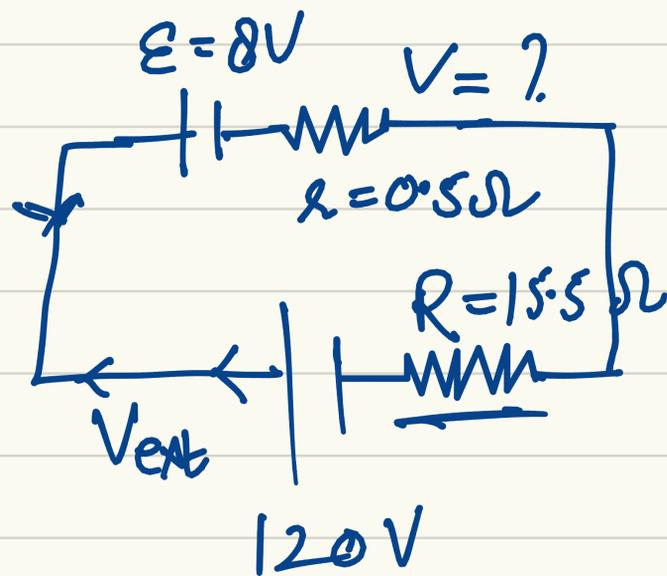

During charging

$$V = E + IR =$$

here

$$I = \frac{V_{\text{net}}}{R + r} = \frac{120 - 8}{15.5 + 0.5}$$

$$I = \frac{112}{16} = 7$$

$$I = 7A$$

Now

$$V = 8 + 7 \times 0.5$$

$$V = 8 + 3.5$$

$$V = 11.5 \text{ volt}$$

A resistor is connected in series ^{Am} to limit the high current and to protect the circuit.

Solⁿ 3.9 Given


$$l = 3 \text{ m}$$

$$A = 2 \times 10^{-6} \text{ m}^2$$

$$I = 3 \text{ A}$$

$$n = 8.5 \times 10^{28} \text{ m}^{-3}$$

$$t = ?$$

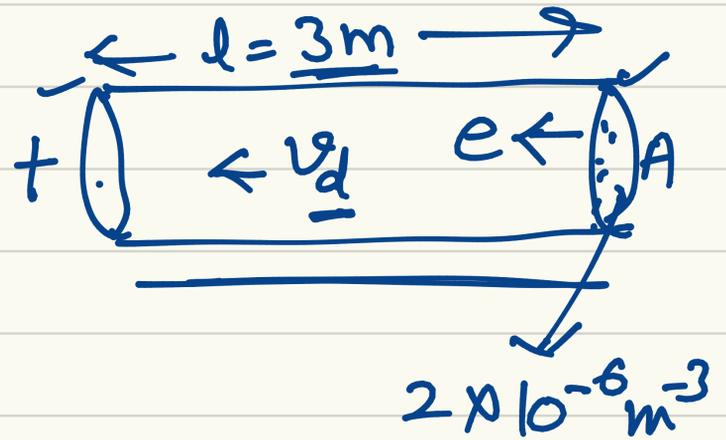

$$\text{by } t = \frac{l}{v_d} = \frac{l}{I/n e A} \quad [I = n e A v_d]$$

$$t = \frac{l n e A}{I}$$

$$= \frac{3 \times 8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6}}{3}$$


$$= 8.5 \times 1.6 \times 2 \times 10^3$$

$$= 17 \times 1.6 \times 10^3$$

$$= 27.2 \times 10^3$$

$$t = 2.7 \times 10^4 \text{ sec}$$

$$= 7.5 \text{ hrs}$$

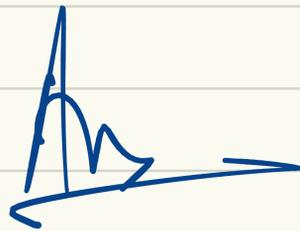

$$\frac{2.7 \times 10^4}{60 \times 60} = 7.5$$