

Example 7.1

Given,

$P = 100 \text{ W}$, $V = 220 \text{ V}$

(a) Resistance $R = \frac{V^2}{P}$

$= \frac{(220)^2}{100} = \frac{48400}{100}$

OR $R = 484 \Omega$ Ans

(b) The peak voltage

$V_m = \sqrt{2} V_{rms}$ [$\because V = V_{rms}$]
 $= 1.414 \times 220$

$= 311 \text{ volt}$ Ans

(c) $I_{rms} = ?$

by $P = VI$

$I_{rms} = \frac{P}{V_{rms}} = \frac{100}{220} = 0.454$

OR $I_{rms} = 0.454 \text{ A}$ Ans

Example 7.2

Given,

$$\text{Inductance } L = 25 \text{ mH} = 25 \times 10^{-3} \text{ H}$$

$$V_{\text{rms}} = 220 \text{ V} \quad \text{frequency } \nu = 50 \text{ Hz}$$

We know

$$\text{Inductive reactance } X_L = \omega L$$

$$= 2\pi \nu L$$

$$= 2 \times 3.14 \times 50 \times 25 \times 10^{-3}$$

$$= 3.14 \times 25 \times 10^{-1}$$

$$X_L = 7.85 \Omega \quad \underline{A_2}$$

$$\text{Now } I_{\text{rms}} = \frac{V_{\text{rms}}}{X_L}$$

$$= \frac{220}{7.85}$$

$$\text{or } I_{\text{rms}} = 28 \text{ A} \quad \underline{A_2}$$

Example 7.3

When the lamp is connected to a capacitor and the capacitor is connected with DC source no current flows in the circuit because

$$\text{Capacitive reactance } X_C = \frac{1}{2\pi \nu C}$$

for d.c frequency $\nu = 0$

then $X_C = \infty$ i.e. current $I = 0$

Therefore no current flows in the circuit even if the capacitance of the capacitor is reduced. Hence lamp will not glow.

Example 7.4

Given

$$C = 15 \mu\text{F} = 15 \times 10^{-6} \text{ F}, V = 220 \text{ Volt}$$

$$\text{frequency } \nu = 50 \text{ Hz}, X_c = ?$$

We know

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi\nu C}$$

$$X_c = \frac{1}{2 \times 3.14 \times 50 \times 15 \times 10^{-6}}$$

$$= \frac{10^6}{314 \times 15} = \frac{10^5}{471}$$

$$= 212 \Omega \quad \underline{\text{Ans}}$$

Now


$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_c}$$

$$= \frac{220}{212} = 1.04 \text{ A} \quad \underline{A_2}$$

$$I_{\text{peak}} = I_m = \sqrt{2} I_{\text{rms}}$$

$$= 1.41 \times 1.04$$

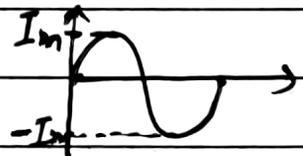
$$= 1.47 \text{ A} \quad \underline{\text{Ans}}$$



i.e. the current oscillates between $+1.47 \text{ A}$ and -1.47 A .

If frequency ν is doubled the capacitive reactance X_c is halved as $X_c = \frac{1}{2\pi\nu C}$ and current I is doubled. [∵ $I = \frac{V}{X_c}$]

Example 7.5

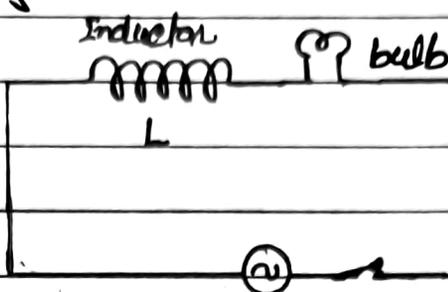

When an iron rod is inserted into the interior of the inductor, inductance L of the coil increases. By $X_L = \omega L$, the ~~same~~ inductive reactance X_L also increases. Therefore, as a result current $I = \frac{V_{rms}}{X_L}$ decreases. Hence the

brightness of the bulb decreases. i.e. the glow of light bulb decreases. Option (b) is correct.

* If AC source is replaced by DC source, the bulb glows more and there will be no effect on inserting iron rod.

Example 7.6

Given,

$$R = 200\Omega, \quad C = 15.0\mu F = 15 \times 10^{-6} F$$


$$V = 220 \text{ Volt}, \quad \nu = 50 \text{ Hz}$$

(a) $I = ?$

We know

$$Z = \sqrt{R^2 + X_C^2}$$
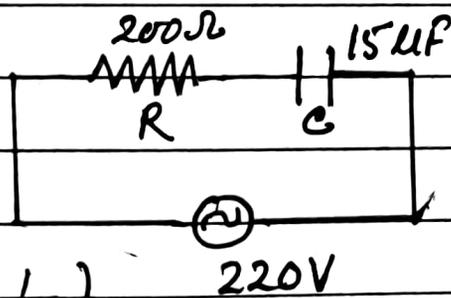
$$= \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} \quad \left[\because X_C = \frac{1}{\omega C} \right]$$



$$Z = \sqrt{R^2 + \left(\frac{1}{2\pi\nu C}\right)^2}$$

$$= \sqrt{(200)^2 + \frac{1}{(2 \times 3.14 \times 50 \times 15 \times 10^{-6})^2}}$$

$$= \sqrt{4 \times 10^4 + (212)^2}$$

$$= \sqrt{4 \times 10^4 + 44944}$$

$$= \sqrt{4 \times 10^4 + 4.5 \times 10^4}$$

$$= 10^2 \sqrt{4 + 4.8}$$

$$= \sqrt{8.8} \times 100$$

$$= 2.915 \times 100$$

$$Z = 291.5 \Omega$$

$$\text{so } I = \frac{V}{Z}$$

$$= \frac{220}{291.5} = 0.755 \text{ A}$$

$$I = 0.755 \text{ A}$$

(b) Since current is same through the circuit, we have

$$V_R = IR = 0.755 \times 200 = 151 \text{ V}$$

$$V_c = IX_c$$

$$= 0.755 \times 212.3$$

$$V_c = 160.3 \text{ V} \quad \underline{A_m}$$

$$\text{here } V_R + V_c = 151 + 160.3$$

$$= 311.3 \text{ V}$$

which is more than source voltage of 220 V. i.e. $V_R + V_c > 220 \text{ V}$

because V_R and V_c are not in same phase. There is a phase difference of $\frac{\pi}{2}$ between V_R and V_c .


Therefore

$$V_{R+c} = \sqrt{V_R^2 + V_c^2}$$

$$= \sqrt{(151)^2 + (160.3)^2}$$

$$= \sqrt{22801 + 25696}$$

$$= \sqrt{48497}$$

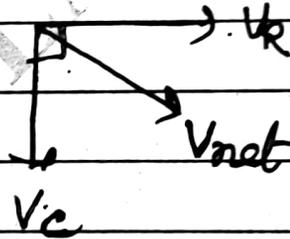

$$V_{R+c} = 220.2 \text{ Volt}$$

$$\approx 220 \text{ V}$$

Thus the phase different between the two voltage should be considered properly to get

or verify $\underline{V_R + V_c = V}$

Example 7.7

(a) Power of an AC circuit is given by

$$P = VI \cos \phi, \quad \cos \phi \rightarrow \text{Power factor}$$

For a given value of P and V

$$I \propto \frac{1}{\cos \phi}$$

i.e. if $\cos \phi$ is small, current I increases.

By $P = I^2 R$, power loss also increases.

So it is clear that low power factor implies large power loss.

(b) We know

$$\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$


$$= \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \quad \left[\because Z \text{ is impedance} \right]$$

As the value of C changes value of Z also changes.

$$\text{for } \cos \phi = 1, \quad \omega L = \frac{1}{\omega C}$$

i.e. power factor $\cos \phi$ can be improved with the help of appropriate value of capacitance C .

II Method

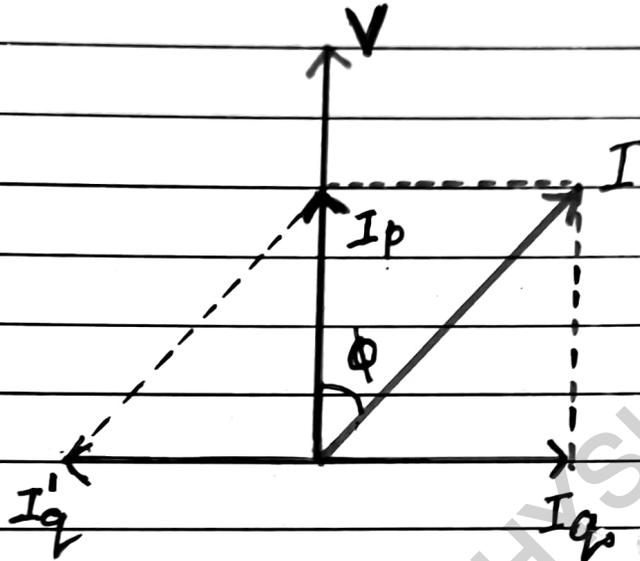

We resolve I into two components. I_p along V and I_q perpendicular to V . As I_q is perpendicular to V , there is no power loss.

$$P = VI \cos \phi$$

for $\phi = 90$, $P = 0$

To improve the power factor I_q must be ~~not~~ neutralise by leading current I_q' .

This can be done by connecting a capacitor of appropriate capacitance in parallel.

Then

$$P = VI_p$$

When capacitor is connected to AC source
by $X_c = \frac{1}{\omega C}$ [current flows and lamp glows]

On reducing the capacitance C , X_c increases.
Therefore lamp will glow less.

JYOTI SHARMA PHYSICS

Example 7.8

Given, $V_0 = 283 \text{ V}$

$$\nu = 50 \text{ Hz}$$

$$R = 3 \Omega$$

$$L = 25.48 \text{ mH} = 25.48 \times 10^{-3} \text{ H}$$

$$C = 796 \mu\text{F} = 796 \times 10^{-6} \text{ F}$$

(a) To find the impedance Z , we first calculate X_L and X_C

$$X_L = 2\pi\nu L$$

$$= 2 \times 3.14 \times 50 \times 25.48 \times 10^{-3} \text{ H}$$

$$= 100 \times 3.14 \times 25.48 \times 10^{-3}$$

$$= 314 \times 25.48 \times 10^{-3}$$

$$= 8000.72 \times 10^{-3}$$

$$X_L = 8 \Omega$$

Now

$$X_C = \frac{1}{2\pi\nu C}$$

$$= \frac{1}{2 \times 3.14 \times 50 \times 796 \times 10^{-6}}$$

$$= \frac{10^6}{314 \times 796}$$

$$= 4 \Omega$$

Therefore

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{3^2 + (8 - 4)^2}$$

$$= \sqrt{9 + 4^2}$$

$$= \sqrt{9 + 16}$$

$$= \sqrt{25}$$

Or $Z = 5 \Omega$



Rough

$796 \approx 800$

1.25×10^3

800×314

$= \frac{1250}{314} = 3.98$

(b) Phase difference, $\phi = \tan^{-1} \frac{X_C - X_L}{R}$

$$\phi = \tan^{-1} \left(\frac{4-8}{3} \right)$$

$$= \tan^{-1} \left(-\frac{4}{3} \right) = \tan^{-1} (-1.33)$$

$$\phi = -53.1^\circ$$

$X_C < X_L$, ϕ is 've' and circuit is predominantly inductive. i.e. current lags the voltage across the source.

(c)

The power dissipated in the circuit

$$P = I^2 R$$

$$\text{here } I_0 = \frac{V_0}{Z} = \frac{283}{5} \text{ so } I = \frac{I_0}{\sqrt{2}} = \frac{1}{\sqrt{2}} \left(\frac{283}{5} \right)$$

$$= \frac{1}{\sqrt{2}} \left(\frac{283}{5} \right) \times \frac{\sqrt{2}}{\sqrt{2}}$$

$$= \frac{283 \sqrt{2}}{10}$$

$$= 28.3 \times 1.414$$

$$= 40.016$$

$$\approx 40 \text{ A}$$

$$\text{Therefore } P = 40^2 \times 3$$

$$= 1600 \times 3$$

$$= 4800 \text{ W } \underline{A_2}$$

(d)

$$\text{Power factor} = \cos \phi = \cos (-53.1^\circ)$$

$$= 0.6 \underline{A_2}$$

Example 7.9

(a) Frequency at which the resonance occurs is

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{where } L = 25.48 \times 10^{-3} \text{ H} \\ C = 796 \times 10^{-6} \text{ F}$$

$$= \frac{1}{\sqrt{25.48 \times 10^{-3} \times 796 \times 10^{-6}}}$$

$$= \frac{1}{\sqrt{25.48 \times 796 \times 10^{-9}}}$$

$$\approx 2.22 \times 10^2$$

$$\text{or } \omega_0 \approx 222 \text{ rad s}^{-1}$$

Now

$$\nu_R = \frac{\omega}{2\pi} = \frac{222}{2 \times 3.14}$$

$$= \frac{222}{6.28}$$

$$\nu_R = 35.35 \text{ Hz} \quad \text{Ans}$$

Rough

$$= \frac{1}{\sqrt{25.45 \times 796 \times 10^{-9}}} \\ \approx \frac{1}{\sqrt{25.5 \times 800 \times 10^{-9}}} \\ = \frac{1}{5 \times 9 \times 10^{-4}} \\ = \frac{10^4}{45} \\ = \frac{10^2}{45} \times 10^2 = 2.22 \times 10^2$$

(b) At resonant condition

$$Z = R = 3 \Omega$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{V_{\text{rms}}}{R} = \frac{203}{\sqrt{2} \times 3}$$

$$\left[\because V_{\text{rms}} = \frac{V_0}{\sqrt{2}} \right]$$

$$\text{or } I_{\text{rms}} = 66.7 \text{ A}$$

The power dissipated at resonance

$$P = I^2 R = (66.7)^2 \times 3$$

$$= 4448.89 \times 3$$

$$= 13346.67$$

$$P \approx 13.35 \text{ kW}$$

* i.e. Power dissipation is more in resonance (than @ 7.8)

Example 7.10

A metal detector works on the principle of resonance in AC circuit.

The doorway has a coil, connected with a capacitor forming an LCR circuit. The circuit is tuned to be in resonance when no metal is present.

When a person with metal walks, impedance of the circuit changes so current also changes. This change is detected and triggers an alarm.

JYOTI SHARMA PHYSICS