

Current Electricity

1. Electric current

$$I = \frac{q}{t} = \frac{\Delta q}{\Delta t} = \frac{ne}{t}$$

charge on one electron
($1.6 \times 10^{-19} e$)
↑
[$q = ne$]
↓ charge → no. of electrons

for conductor of length 'l' and cross-section area A

$$q = (ne)(Al)$$

Unit of q → coulomb (C)

2. Instantaneous current

$$I = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$

Unit of I → Ampere (A)

also $\int dq = \int I dt$
or $q = \int I dt$

3. Ohm's law

$$R = \frac{V}{I} = \text{Constant}$$

R → Resistance
V → Potential diff.

4. Resistance (R)

$$R = \frac{\rho l}{A}$$

ρ → Resistivity
l → length of conductor
A → cross-section area of conductor

Unit of R → Ohm (Ω)

5. Resistivity (ρ)

$$\rho = \frac{RA}{l}$$

Unit of ρ → Ohm-m ($\Omega\text{-m}$)

* Resistivity ρ does not depend on l & A of the conductor

$$\frac{R_1 A_1}{l_1} = \frac{R_2 A_2}{l_2}$$

[For two wires of same material]

OR $\frac{R_1}{R_2} = \frac{l_1}{l_2} \cdot \frac{A_2}{A_1}$

6. When shape of wire is changed
 volume of wire does not change

$$V_1 = V_2$$

$$A_1 l_1 = A_2 l_2$$

@jyotisharmaphysics

$$\text{or } \frac{l_1}{l_2} = \frac{A_2}{A_1}$$

7. current density (J)

$$J = \frac{I}{A} \Rightarrow I = \vec{J} \cdot \vec{A} = \int A \cdot \vec{J} \cdot d\vec{S}$$

Unit of $J \rightarrow \text{Am}^{-1}$

8. Ohm's law in vector form

$$\vec{J} = \sigma \vec{E}$$

here $\sigma = \frac{ne^2 \tau}{m}$ conductivity

@jyotisharmaphysics

$$\text{or } \vec{E} = \vec{J} \rho$$

$$[\because \sigma = \frac{1}{\rho}]$$

unit of $\sigma \rightarrow \Omega^{-1} \text{m}^{-1}$ or Sm^{-1} Siemens

9. Drift velocity U_d

$$U_d = \frac{eE \tau}{m}$$

$E \rightarrow$ Electric field,
 $\tau \rightarrow$ Relaxation time

vector form $\vec{U}_d = -\frac{eE \tau}{m}$

-ve sign shows the
 opposite dirⁿ of \vec{U}_d & \vec{E}

unit of $U_d \rightarrow \text{ms}^{-1}$

10. Relation b/w drift velocity and current

$$I = neAU_d$$

$n \rightarrow$ electron no. density

11. Mobility μ

$$\mu = \frac{U_d}{E} = \frac{e \tau}{m}$$

unit of $\mu \rightarrow \text{m}^2 \text{V}^{-1} \text{s}^{-1}$

12. Temperature dependence of Resistivity

@jyotisharmaphysics

$$\rho_T = \rho_0 [1 + \alpha (T - T_0)] \quad T_0 \rightarrow \text{Reference temp.}$$

also

$$\rho_2 = \rho_1 [1 + \alpha (T_2 - T_1)]$$

$\alpha \rightarrow$ temperature coefficient of resistivity

$$\alpha = \frac{\rho_T - \rho_0}{\rho_0 \Delta T} \quad [\Delta T = T - T_0]$$

For resistance

$$R_T = R_0 [1 + \alpha (T - T_0)]$$

and $\alpha = \frac{R_2 - R_1}{R_1 \Delta T}$

Unit of α $^{\circ}\text{C}^{-1}$

* For unknown temp. if resistance at that temp. is given

$$T = \frac{R_{100} - R_0}{R_T - R_0} \times 100$$

13. Electric Energy (E)

$$E = P \times t$$

$$E = I^2 R t$$

$$E = \frac{V^2}{R} t$$

$E \rightarrow$ Energy \rightarrow in joule (J)

$P \rightarrow$ Power \rightarrow in watt (W)

$t \rightarrow$ time \rightarrow in second (s)

$V \rightarrow$ voltage \rightarrow in volt (V)

$R \rightarrow$ Resistance \rightarrow in ohm (Ω)

@jyotisharmaphysics

14. Electric Power (P)

$$P = VI$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$


* Power dissipated $P_c = \frac{P^2}{V^2} R$

15. Combination of resistances -

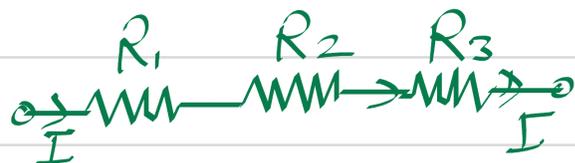(i) In series (I constant)


$$R_s = R_1 + R_2 + R_3 + \dots$$

$R_s \rightarrow$ equivalent resistance in series



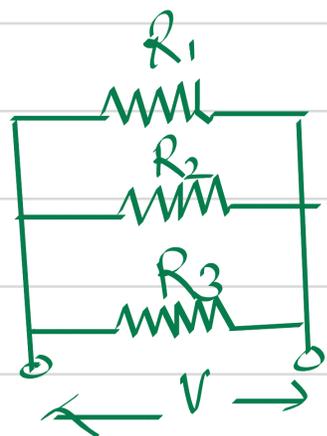(ii) In parallel (V constant)

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



@jyotisharmaphysics

* For n identical resistors

$$R_s = nR$$

$$R_p = \frac{R}{n}$$

16. Terminal voltage of an electric cell

$$V = \mathcal{E} - IR \quad [\text{In closed circuit}]$$

$V \rightarrow$ Terminal voltage in volt (V)

$\mathcal{E} \rightarrow$ emf of cell in volt (V)

$R \rightarrow$ Internal resistance of cell in ohm (Ω)

@jyotisharmaphysics

here $V = IR$, then

$$IR = \mathcal{E} - IR$$

or


$$I = \frac{\mathcal{E}}{R + R}$$

* When cell is charging

$$V = \mathcal{E} + IR$$

Grouping of Cells

(I) In Series

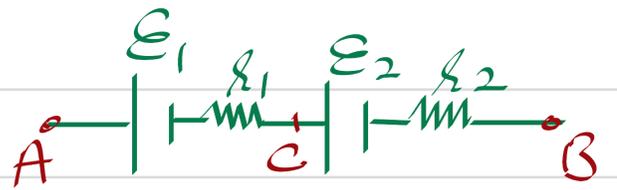

$$\mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2$$

[\mathcal{E}_{eq} → Equivalent emf]

$$r_{eq} = r_1 + r_2$$


[r_{eq} → Equivalent resistance]

For n identical cells $\mathcal{E}_{eq} = n\mathcal{E}$

$r_{eq} = nr$

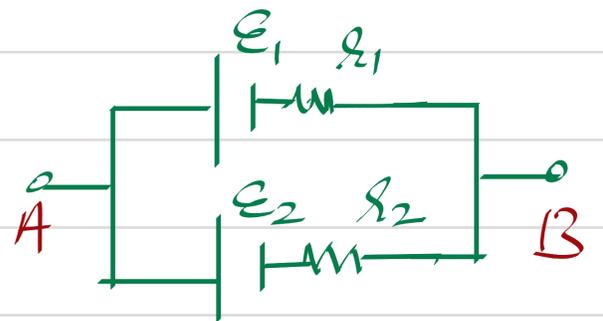(II) In Parallel

$$\frac{\mathcal{E}_{eq}}{r_{eq}} = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2}$$




$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2}$$

For n identical cell $\mathcal{E}_{eq} = \mathcal{E}$, $r_{eq} = \frac{r}{n}$

17. Kirchhoff's Rule

(I) Junction Rule

$$\sum I = 0$$

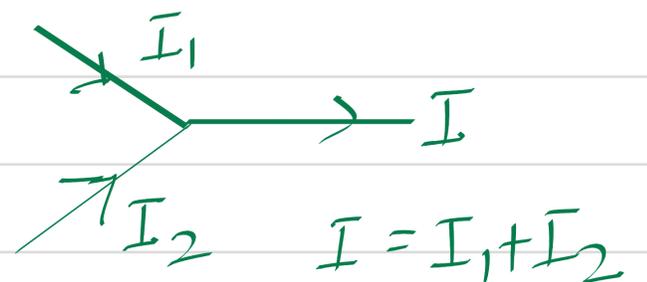

(II) Loop Rule

$$\sum V = 0$$

$$\text{or } \sum V_{\text{source}} - \sum IR = 0$$

$$\text{or } \sum V_{\text{source}} = \sum IR$$

18. Condition of Balanced Wheatstone Bridge

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow \frac{R_1}{R_3} = \frac{R_2}{R_4}$$

