

# Current Electricity

## NCERT Examples

Date   /  /    
Ch. 3

Example 3.1

Estimate the

drift motion.

Solution:-

Given -

$$A = 1 \times 10^{-7} \text{ m}^2$$

$$I = 1.5 \text{ A}$$

No of atoms = no of electrons

Atomic mass of Copper = 63.5 u

Density of Copper =  $9 \times 10^3 \text{ kg/m}^3$

$V_d = ?$

$$I = n e A V_d$$

$$V_d = \frac{I}{n e A}$$

For n

We know

$$\text{No of atom in } 63.5 \text{ g} = 6 \times 10^{23}$$

$$\text{No of atom in } 1 \text{ g} = \frac{6 \times 10^{23}}{63.5}$$

$$\text{'' '' '' } 9 \times 10^6 \text{ g} = \frac{6 \times 10^{23}}{63.5} \times 9 \times 10^6$$

$$n = \frac{6 \times 9 \times 10^{29}}{63.5}$$

$$= \frac{5400}{63.5} \times 10^{28}$$

$$\begin{array}{r} 8.5 \\ 127 \overline{) 1080} \\ \underline{1016} \\ 640 \\ \underline{635} \\ 5 \end{array}$$

$$n = 8.5 \times 10^{28} \text{ m}^{-3}$$

$$V_d = \frac{I}{n e A} = \frac{1.5}{8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 10^{-7}}$$

$$V_d = \frac{150 \times 10^{-28+19+7}}{85 \times 16}$$

$$V_d = \frac{30 \times 150 \times 10^{-2}}{85 \times 16} = \frac{30 \times 10^{-2}}{16 \times 17} = \frac{30 \times 10^{-2}}{272}$$

$$V_d = \frac{300 \times 10^{-3}}{272} \quad \begin{array}{r} 272 \overline{) 300} \quad (1.1) \\ \underline{272} \\ 280 \end{array}$$

$$V_d = 1.1 \times 10^{-3} \text{ m/s}$$

$$V_d = 1.1 \text{ mm s}^{-1} \text{ Ans}$$

(b)

$$\frac{V_{drift}}{V_{thermal}} = ?$$

For  $V_{thermal}$ 

$$\frac{1}{2} m v^2 = \frac{3}{2} k_B T$$

$$v^2 = \frac{3 k_B T}{m}$$

For  $m$ 

$$\text{Mass of } 6 \times 10^{23} \text{ atoms} = 63.5 \text{ g}$$

$$\text{So mass of one atom} = \frac{63.5}{6 \times 10^{23}} \text{ g}$$

$$= \frac{63.5 \times 10^{-3}}{6 \times 10^{23}} \text{ kg}$$

$$v^2 = \frac{3 k_B T}{m} = \frac{1.38 \times 10^{-23} \times 300 \times 6 \times 10^{23}}{63.5 \times 10^{-3}}$$

$$= \frac{1.38 \times 300 \times 6 \times 10^3}{63.5} \quad [T = 27^\circ\text{C} + 273 = 300\text{K}]$$

$$= \frac{138 \times 18 \times 10^5}{635}$$

$$v^2 = \frac{138 \times 18 \times 10^4}{635}$$

$$v^2 = \frac{2484 \times 10^4}{635}$$

$$\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$$R_t = R_0 (1 + \alpha \Delta T)$$

$$\text{or } R_t - R_0 = R_0 \alpha \Delta T$$

$$\text{or } R_2 - R_1 = R_1 \alpha \Delta T$$

$$\Delta T = \frac{R_2 - R_1}{R_1 \alpha}$$

$$= \frac{85.8 - 75.3}{75.3 \times 1.70 \times 10^{-4}}$$

$$= \frac{10.5 \times 10^4}{75.3 \times 1.70}$$

$$\Delta T = \frac{105 \times 10^4}{1280.1}$$

$$= \frac{1050 \times 10^2}{128}$$

$$\Delta T = 8.2 \times 10^2$$

$$\text{or } T_2 - T_1 = 820$$

$$T_2 = 820 + T_1$$

$$T_2 = 820 + 27$$

$$= 847^\circ\text{C} \text{ Ans}$$

Thus the steady temperature of the nichrome element =  $847^\circ\text{C}$

### Example-3.4

The resistance ----- of the bath.

Solution  $\Rightarrow$

Given  $\rightarrow$

$$\text{Ice point } T_1 = 0^\circ\text{C}$$

$$\text{Steam point } T_2 = 100^\circ\text{C}$$

$$R_0 = 5 \Omega$$



$$= \frac{0.795}{0.23} \times 100$$

$$= \frac{79.3}{23} \times 10^2$$

$$= 3.456 \times 10^2$$


$$t = 345.6^\circ\text{C}$$

Thus the temperature of the bath is  
345.65°C Ans

Example 3.5 (Not in new syllabus)

A Network - - - - - the voltage drop

Solution:-

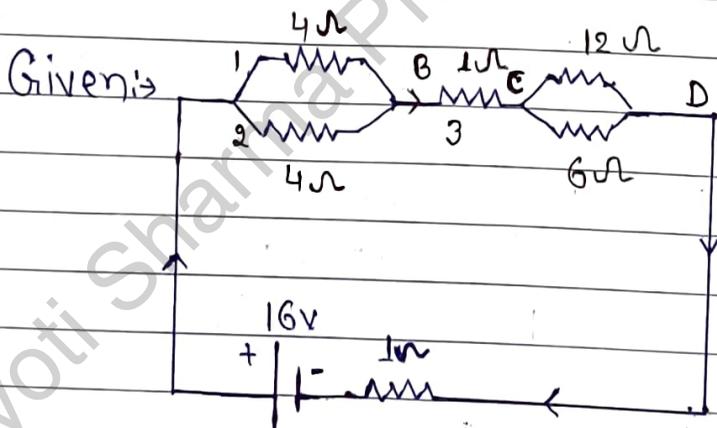

Let the resistances are given as

$$R_1 = R_2 = 4\Omega, \quad R_3 = 1\Omega$$

$$R_4 = 12\Omega \text{ and } R_5 = 6\Omega$$

and the internal resistance of the battery  $r = 1\Omega$

emf of the battery = 16V

From fig.

$R_1$  and  $R_2$  are in parallel. Therefore.

$$R_{12} = \frac{R_1 R_2}{R_1 + R_2} = \frac{4 \times 4}{4 + 4} = \frac{16}{8} = 2\Omega$$

$$R_{12} = 2 \Omega$$

$R_4$  and  $R_5$  are also in  $\parallel$ . Therefore

$$R_{45} = \frac{R_4 R_5}{R_4 + R_5} = \frac{12 \times 6}{12 + 6} = \frac{72}{18} = 4$$

or  $R_{45} = 4 \Omega$

Now  $R_{12}$ ,  $R_3$  and  $R_{45}$  are in series. Therefore

$$R_{12345} = 2 + 1 + 4$$

$$= 7 \Omega$$



Now the  $1 \Omega$  is also in series.

So

$$R_{eq} = R_{12345} + 1$$

$$= 7 + 1$$

$$R_{eq} = 8 \Omega \text{ Ans}$$

(b) The total current  $I$  in the circuit

$$I = \frac{E}{R + r} = \frac{E}{R_{eq}} = \frac{16}{8} = 2$$


or  $I = 2 \text{ A}$

Let the current through  $4 \Omega$  and  $4 \Omega$  is  $I_1$  and  $I_2$ , As  $4 \Omega$  are in parallel, we have

$$I_1 R_1 = I_2 R_2$$

or  $\frac{I_1}{I_2} = \frac{R_2}{R_1} = \frac{4}{4} = 1$

$$\text{Or } I_1 = I_2$$

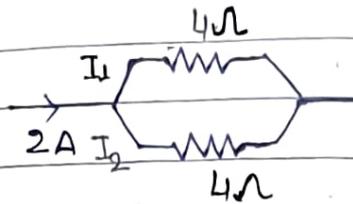

also we have

$$I_1 + I_2 = 2A$$

$$\text{Hence } I_1 = I_2 = 1A$$

Now current through  $1\Omega$ , between BC

$$I_3 = 2A$$

Now consider that the current is  $I_4$  in  $12\Omega$  resistor and  $I_5$  through  $6\Omega$  resistor. These resistors are in parallel. Therefore

$$I_4 R_4 = I_5 R_5$$

$$\text{Or } \frac{I_4}{I_5} = \frac{R_5}{R_4} = \frac{6}{12} = \frac{1}{2}$$

$$\text{Or } I_5 = 2I_4$$

also we have

$$I_4 + I_5 = 2A$$

$$\text{Or, } I_4 + 2I_4 = 2A$$


$$\text{Or, } 3I_4 = 2A$$

$$I_4 = \frac{2}{3}A$$

$$\text{and } I_5 = 2I_4$$

$$= 2 \times \frac{2}{3}A$$

$$\text{Or } I_5 = \frac{4}{3}A$$

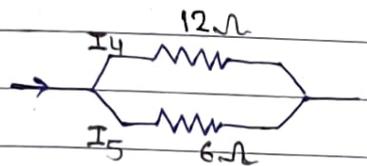

Hence

- |  |              |
|--|--------------|
| → Current through $4\Omega$ and $4\Omega = 1A$ | } <u>Ans</u> |
| → Current through $1\Omega = 2A$               |              |
| → Current through $12\Omega = \frac{2}{3}A$    |              |
| → Current through $6\Omega = \frac{4}{3}A$     |              |


$$\checkmark_{\text{ISTA}} \rightarrow \text{Current through } 6\Omega = \frac{4}{3}A$$

Current through  $6\ \Omega = \frac{4}{3}\ \text{A}$

(c)


Voltage drops
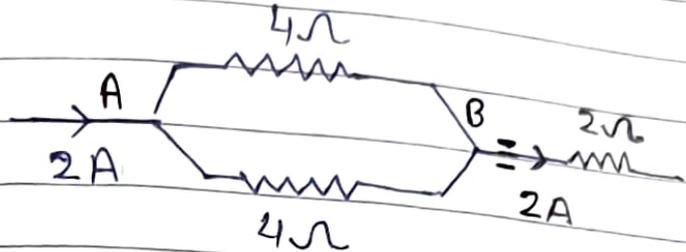
$$\begin{aligned} \rightarrow V_{AB} &= IR \\ &= 2 \times 2 \\ &= 4\ \text{V} \end{aligned}$$



$$\begin{aligned} \rightarrow V_{BC} &= 2 \times 1 \\ &= 2\ \text{V} \end{aligned} \quad \text{[By } V = IR\text{]}$$
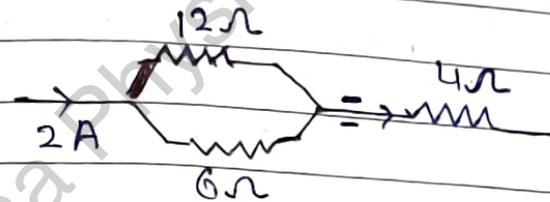
$$\begin{aligned} \rightarrow V_{CD} &= 2 \times 4 \\ &= 8\ \text{V} \end{aligned}$$



$\Rightarrow$  Hence  $V_{AB} = 4\ \text{V}$   
 $V_{BC} = 2\ \text{V}$   
 $V_{CD} = 8\ \text{V}$


Ans

\*  $V_{AD} = V_{AB} + V_{BC} + V_{CD} = 4 + 2 + 8 = 14\ \text{V}$   
 but  $\text{EMF} = 16\ \text{V}$ . The loss of  $2\ \text{V}$  is by the internal resistance of  $1\ \Omega$ .

Example 3.6 <sup>5</sup>

A battery of ----- of the Cube

Solution

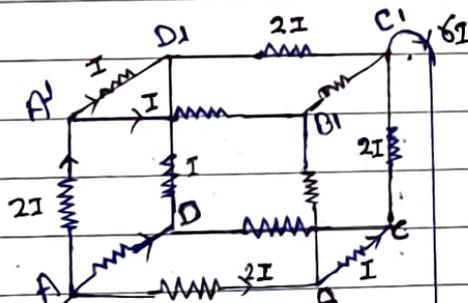

Let a current of magnitude  $6I$  enter at A and leave at C'. Here all the resistors are of  $1\Omega$ . Therefore we use symmetry for the distribution of current.

By apply Kirchhoff's II rule in loop ABC C'E

$$-2I \times 1 - I \times 1 - 2I \times 1 + 10 = 0$$

$$-5I = -10$$

$$\text{or } I = 2 \text{ A}$$

$$\therefore 6I = 12 \text{ A}$$

$$R_{eq} = \frac{V}{6I} =$$

$$= \frac{10}{12} = \frac{5}{6}$$

$$R_{eq} = \frac{5}{6} \Omega \text{ Ans}$$

\* The current flowing along each


$$\text{edge} = 2I = 2 \times 2 = 4$$

$$2I = 4 \text{ A Ans}$$

Example - 3.76

Determine - - - - - Shown in fig.

Solution  $\rightarrow$

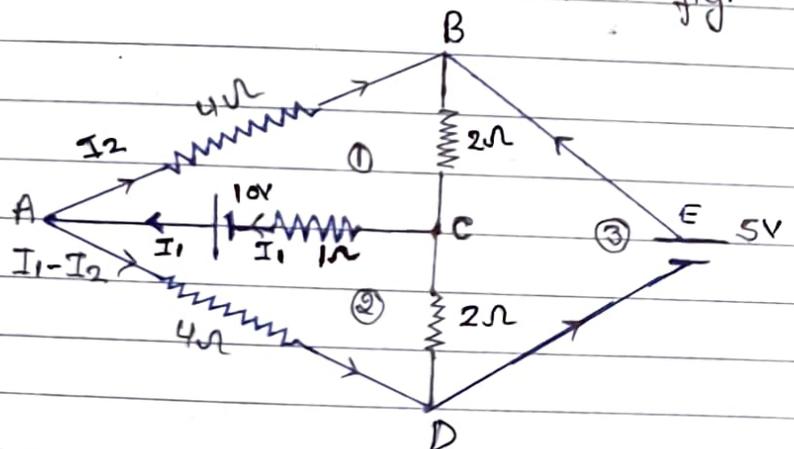

Here we have three unknowns  $I_1$ ,  $I_2$  and  $I_3$ . We apply second rule (loop rule) of Kirchhoff to three different loops to find the value of unknown currents.

In loop ①

$$-4I_2 - 2(I_2 + I_3) - I_1 + 10 = 0$$

$$\text{or } I_1 + 4I_2 + 2(I_2 + I_3) = 10$$

$$\text{or } I_1 + 6I_2 + 2I_3 = 10 \quad \text{--- (1)}$$

In loop ②

$$-4(I_1 - I_2) + 2(I_2 + I_3 - I_1) - I_1 + 10 = 0$$

$$\text{or } -7I_1 + 6I_2 + 2I_3 = -10$$

$$7I_1 - 6I_2 - 2I_3 = 10 \quad \text{--- (2)}$$

In loop ③

$$-2(I_2 + I_3) - 2(I_2 + I_3 - I_1) + 5 = 0$$

$$\text{or } 2 \times (I_2 + I_3) + 2(I_2 + I_3 - I_1) - 5 = 0$$

$$\text{or } -2I_1 + 4I_2 + 4I_3 = 5 \quad \text{--- (3)}$$

eqn ① + ② we get

$$8I_1 = 20$$

$$\text{or } I_1 = \frac{20}{8} \quad \text{or } \boxed{I_1 = \frac{5}{2} \text{ A}}$$

Now ①  $\times 2$  - ③

$$2I_1 + 12I_2 + 4I_3 = 20$$

$$-2I_1 + 4I_2 + 4I_3 = 5$$

$$\begin{array}{r} + \\ \hline 4I_2 = 15 \end{array}$$

$$\text{put } I_1 = \frac{5}{2} \Rightarrow 4 \times \frac{5}{2} + 8I_2 = 15$$

$$10 + 8I_2 = 15$$

$$8I_2 = 5 \Rightarrow \boxed{I_2 = \frac{5}{8} \text{ A}}$$

$$I_2 = \frac{5}{8} A$$

Now from eqn ①

$$I_1 + 6I_2 + 2I_3 = 10$$

$$\frac{5}{2} + 6 \times \frac{5}{8} + 2I_3 = 10$$

$$2I_3 = 10 - \frac{5}{2} - \frac{30}{8}$$

$$= \frac{80 - 20 - 30}{8}$$

$$2I_3 = \frac{30}{8}$$

$$I_3 = \frac{15}{8} A$$

$$\# I_1 = \frac{5}{2} A$$

$$\# I_2 = \frac{5}{8} A$$


$$\# I_3 = \frac{15}{8} A$$

Ans

Example - 3.8 7

The four arms ----- resistances.

Solution:  $\Rightarrow$

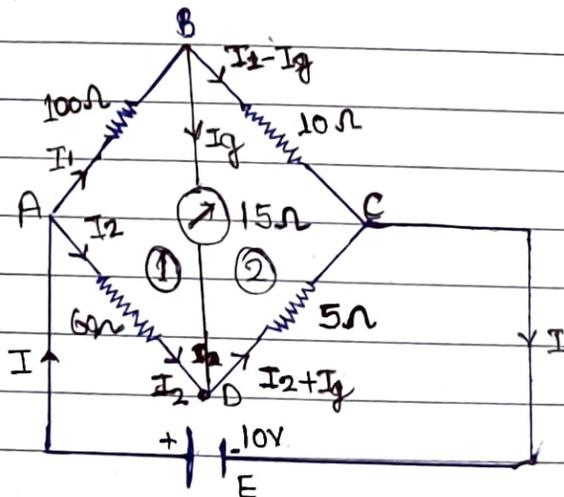

By KVR  
In loop ①  $\begin{cases} \Sigma V = 0 \\ \Sigma IR = 0 \end{cases}$

$$100I_1 + 15I_g - 60I_2 = 0$$

$$\text{or } 20I_1 + 3I_g - 12I_2 = 0 \quad \text{--- (I)}$$

In loop ②

$$15I_g + 5(I_2 + I_g) - 10(I_1 - I_g) = 0$$

$$15I_g + 5I_2 + 5I_g - 10I_1 + 10I_g = 0$$

$$30I_g + 5I_2 - 10I_1 = 0$$

$$6I_g + I_2 - 2I_1 = 0 \quad \text{--- (II) OR } -2I_1 + 6I_g + I_2 = 0$$

Now in loop ③

$$\rightarrow 60I_2 + 5(I_2 + I_g) - 10 = 0$$

$$\rightarrow \text{or } 60I_2 + 5I_2 + 5I_g = 10$$

$$\rightarrow 65I_2 + 5I_g = 10$$

$$\text{or } 13I_2 + I_g = 2 \quad \text{--- (III)}$$

eqn ① + 10 × eqn ②

$$\rightarrow 20I_1 + 3I_g - 12I_2 = 0 \quad \text{--- (I)}$$

$$\rightarrow -20I_1 + 60I_g + 10I_2 = 0 \quad \text{--- (II)}$$

$$+ \quad \hline 63I_g - 2I_2 = 0$$

$$\Rightarrow I_2 = \frac{63}{2} I_g$$

From eqn ③

$$\Rightarrow 13I_2 + I_g = 2$$

$$\Rightarrow 13 \times \frac{63}{2} I_g + I_g = 2$$

$$\Rightarrow \frac{819}{2} I_g + I_g = 2 \Rightarrow 409.5 I_g + I_g = 2$$

$$\Rightarrow 410.5 I_g = 2$$

$$\Rightarrow 410.5 I_g = 2$$

$$\Rightarrow I_g = \frac{2}{410.5} = 0.00487 A$$

$$\Rightarrow \text{Or } \boxed{I_g = 4.87 \text{ mA}} \quad \text{Am}$$

Jyoti Sharma Physics